

In the name of God

Digital Electronics

CA2

Mohammad Yahyapour

Part 1: Design

We define the **Inverter**, **AND**, and **OR** circuits as subcircuits, and then, using these gates, we define the **XOR** circuit.

```
*****Inverter*****
.subckt    INV      Vin      Vout
M1        Vout     Vin      0      0      nch_lvt      l=Lmin      w=Wn
M2        Vout     Vin      VD     VD     pch_lvt      l=Lmin      w='2*Wn'
Vsupply    VD      0      VDD
.ends      INV
```

Figure 1: inverter code

```
*****2-Input-Nand*****
.subckt    NAND2    A        B        Vout
M1        x        B        0        0      nch_lvt      l=Lmin      w='2*Wn'
M2        Vout     A        x        0      nch_lvt      l=Lmin      w='2*Wn'
M3        Vout     A        VD     VD     pch_lvt      l=Lmin      w='2*Wn'
M4        Vout     B        VD     VD     pch_lvt      l=Lmin      w='2*Wn'
Vsupply    VD      0      VDD
.ends      NAND2

*****2-Input-And*****
.subckt    AND2      A        B        Vout
X1        A        B        out0      NAND2
X2        out0     Vout     INV
.ends      AND2
```

Figure 2 And code

```
*****2-Input-NOR*****
.subckt    NOR2      A        B        Vout
M1        Vout     A        0        0      nch_lvt      l=Lmin      w=Wn
M2        Vout     B        0        0      nch_lvt      l=Lmin      w=Wn
M3        x        A        VD     VD     pch_lvt      l=Lmin      w='4*Wn'
M4        Vout     B        x        VD     pch_lvt      l=Lmin      w='4*Wn'
Vsupply    VD      0      VDD
.ends      NOR2
```

Figure 3 And code

```

**** 2-input xor gate ****
.subckt XOR2 A B Vout
X1 A Abar INV
X2 B Bbar INV

X3 Abar B out0 AND2
X4 A Bbar out1 AND2
X5 out0 out1 Vout OR2
.ends XOR2

```

Figure 4 XOR code

```

*****GP-Logic*****
.subckt GP A B G P
X1 A B G AND2
X2 A B P XOR2
.ends GP

```

Figure 5 GP code

 


Figure 6 GP logic

```

*****A021-Logic*****
.subckt A021 A B C Vout
X1 B C out0 AND2
X2 A out0 Vout OR2
.ends A021

```

Figure 7 A021 code

 


Figure8 Logic A021

A	B	C	C +1	Condition
0	0	0	0	No Carry Generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No Carry Propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	Carry Generate
1	1	1	1	

Figure 9 CLA truth table

The **carry lookahead adder** is designed to speed up the transfer of carry to the next blocks. For this reason, it examines different cases for each index, such as the possible values of A_i , B_i , and C_{in} , and whether a carry bit will be generated or not. For example, when both bits A_i and B_i are equal to 1, a generate bit is produced without considering any previous carry bits. In another example, if one of these bits is 1 and the other is 0, then if C_{in} is 1, a carry bit is produced through **propagation**, meaning it is passed from the previous blocks. Now, the given expression will be analyzed.

$$G_{4:1} = G_4 + P_4 \cdot G_3 + P_4 \cdot P_3 \cdot G_2 + P_4 \cdot P_3 \cdot P_2 \cdot G_1 + P_4 \cdot P_3 \cdot P_2 \cdot P_1 \cdot G_0$$

Now, based on the explanations above, all the cases in which the carry bit $G_{4:1}$ is generated are listed:

1. G_4 is generated on its own.
2. G_3 is generated, and P_4 propagates it.
3. G_2 is generated, P_3 propagates it, and finally P_4 also propagates it.
4. G_1 is generated, and P_2 , P_3 , and P_4 propagate it.
5. G_0 is generated, and P_2 , P_1 , P_3 , and P_4 propagate it all the way to the output.

Part 2: Vector Test

```

1  ; specifies # of bits associated with each vector
2  radix 1 4 4 1 4
3  ; *****
4  ; defines name for each vector. For multi-bit vectors,
5  ; innermost [] provide the bit index range, MSB:LSB
6  vname Cin A[4:1] B[4:1] Cout S[4:1]
7  ; *****
8  ; defines vector as input, output, or bi-directional
9  io i i i o o
10 ; defines time unit
11 tunit ns
12 slope 0.001
13 PERIOD 0.8
14 ODELAY 0.75
15 ; *****
16 vih 1 1 F F 0 0
17 vil 0 1 F F 0 0
18 voh 0.85 0 0 0 1 F
19 vol 0.15 0 0 0 1 F
20 ; tabular data section
21 0 0 0 0 0
22 0 2 1 0 3
23 0 4 2 0 6
24 0 6 3 0 9
25 0 9 5 0 E
26 0 B 5 1 0
27 0 A 6 1 0
28 0 A A 1 4
29 0 F F 1 E
30 1 5 6 0 C

```

Figure 10 VEC_CLA4bit.txt

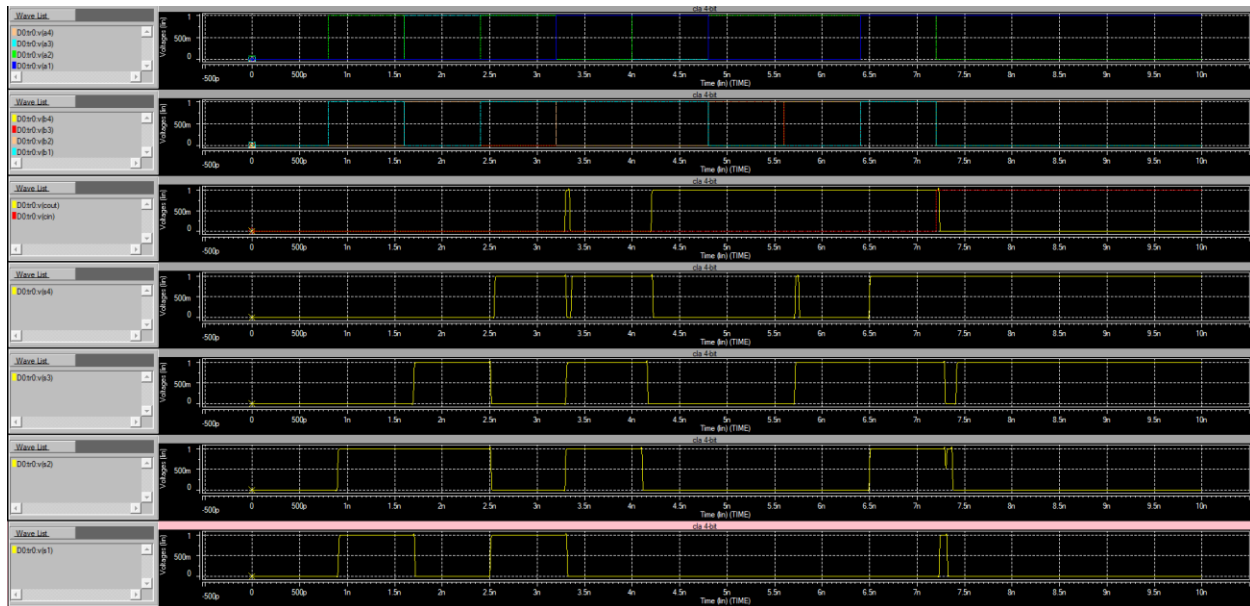


Figure 11 VEC_CLA4bit.txt input and output

The file **VEC_CLA4bit.txt** was used to provide the inputs.

Part 3: Delay and Power

For the delay section, a separate file named **part3.txt** was used to provide the inputs.

```
***** transient analysis tnom= 25.000 temp= 25.000 *****
td_tb1_cout= 205.0131p targ= 1.0055n trig= 800.5000p
td_tb1_s4= 220.3126p targ= 1.0208n trig= 800.5000p
td_tb1_s3= 166.6639p targ= 967.1639p trig= 800.5000p
td_tb1_s2= 112.9615p targ= 913.4615p trig= 800.5000p
td_tb1_s1= 115.4398p targ= 915.9398p trig= 800.5000p
td_tb2_s4= 117.8598p targ= 1.7184n trig= 1.6005n
td_tb3_s4= 207.1672p targ= 3.4077n trig= 3.2005n
td_tb4_cout= 152.5850p targ= 4.9531n trig= 4.8005n
td_tb4_s4= 167.5396p targ= 4.9680n trig= 4.8005n
td_tb4_s3= 113.9279p targ= 4.9144n trig= 4.8005n
td_tb4_s2= 113.9024p targ= 4.9144n trig= 4.8005n
td_tb4_s1= 110.6091p targ= 4.9111n trig= 4.8005n

***** job concluded
```

Figure 12 Delays at a temperature of 25 °C.

```
***** transient analysis tnom= 25.000 temp= 0.000 *****
td_tb1_cout= 199.2170p targ= 999.7170p trig= 800.5000p
td_tb1_s4= 214.3158p targ= 1.0148n trig= 800.5000p
td_tb1_s3= 162.1069p targ= 962.6069p trig= 800.5000p
td_tb1_s2= 109.8725p targ= 910.3725p trig= 800.5000p
td_tb1_s1= 112.2505p targ= 912.7505p trig= 800.5000p
td_tb2_s4= 114.5208p targ= 1.7150n trig= 1.6005n
td_tb3_s4= 200.3497p targ= 3.4008n trig= 3.2005n
td_tb4_cout= 148.1115p targ= 4.9486n trig= 4.8005n
td_tb4_s4= 163.0096p targ= 4.9635n trig= 4.8005n
td_tb4_s3= 110.6850p targ= 4.9112n trig= 4.8005n
td_tb4_s2= 110.8125p targ= 4.9113n trig= 4.8005n
td_tb4_s1= 107.6391p targ= 4.9081n trig= 4.8005n

***** job concluded
```

Figure 13 Delays at a temperature of 0 °C.

```
***** transient analysis tnom= 25.000 temp= 100.000 *****
td_tb1_cout= 223.2959p targ= 1.0238n trig= 800.5000p
td_tb1_s4= 238.9275p targ= 1.0394n trig= 800.5000p
td_tb1_s3= 180.8903p targ= 981.3903p trig= 800.5000p
td_tb1_s2= 122.6669p targ= 923.1669p trig= 800.5000p
td_tb1_s1= 124.5833p targ= 925.0833p trig= 800.5000p
td_tb2_s4= 128.3040p targ= 1.7288n trig= 1.6005n
td_tb3_s4= 225.6382p targ= 3.4261n trig= 3.2005n
td_tb4_cout= 166.4517p targ= 4.9670n trig= 4.8005n
td_tb4_s4= 182.1402p targ= 4.9826n trig= 4.8005n
td_tb4_s3= 124.1409p targ= 4.9246n trig= 4.8005n
td_tb4_s2= 123.4960p targ= 4.9240n trig= 4.8005n
td_tb4_s1= 119.5401p targ= 4.9200n trig= 4.8005n

***** job concluded
```

Figure 14 Delays at a temperature of 100 °C.

As observed in Figures 11 to 13, the delays increase with rising temperature. This is because the circuit resistance increases, and the **Elmore delay**, which is based on RC, reflects this effect.

 


Figure 15 Delay of A1 to S3

At a temperature of 25 °C, it takes approximately **0.21 nanoseconds**, which is close to **0.205 ns**.

 


Figure 16 Delay of A1 to S3

At a temperature of 25 °C, it takes approximately **0.167 nanoseconds**, which is close to **0.166 ns**.

In this section, we calculate the **power consumption** as requested. Therefore, the file **part3_power.txt** is used to provide the inputs, and the corresponding file for this section has been placed in the **power version** folder.

```
avgpower= 175.8785u  from= 0.  to= 4.0000n
```

Figure 16 Power at a temperature of 0 °C.

```
avgpower= 182.3196u  from= 0.  to= 4.0000n
```

Figure 17 Power at a temperature of 25 °C.

```
avgpower= 214.1631u  from= 0.  to= 4.0000n
```

Figure 18 Power at a temperature of 100 °C.

As can be seen, power consumption also increases with rising temperature. This is because most of the power is consumed during switching, and as the switching time increases, power consumption also increases.